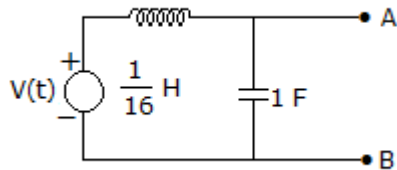


CORRECTIONS/ERRATA: ELECTRONICS

The circuit in figure will act as ideal current source with respect to terminals A and B when frequency is:



- A. 0
- B. 1 rad/sec
- C. 4 rad/sec – Ans.
- D. 16 rad/sec

Not B.

In a shunt-shunt negative feedback amplifier, as compared to the basic amplifier:

- A. both input and output impedances decrease - Ans.
- B. input impedance decrease but output impedance increase
- C. I/P impedance increases but O/P impedance decreases
- D. both input and O/P impedance increase

Not B.

Generally, the gain of a transistor amplifier falls at high frequencies due to the:

- A. internal capacitance of the device - Ans.
- B. coupling capacitor at the input
- C. skin effect
- D. coupling capacitor at the output

Not B.