



Answers & Solutions:

1. **A. electrons**
2. **C. the EB junction must be forward-biased and the CB junction must be-biased.**

3. **B. a stable Q point**

4. **A. 1.25 A**

Solution:

$$I_E = I_B + I_C$$

$$I_E = 50 \text{ mA} + 1.2 \text{ A}$$

$$I_E = 1.25 \text{ A} \rightarrow \text{Ans.}$$

5. **D. the arrow points in on the emitter lead.**

6. **B. I_E .**

7. **A. 361.6 k Ω ; 2.4 k Ω**

Solution:

$$I_B = \frac{I_C}{\beta} = \frac{2.5 \text{ mA}}{80} = 31.25 \mu\text{A}$$

$$R_B = \frac{V_{RB}}{I_B} = \frac{V_{CC} - V_{BE}}{I_B} = \frac{12 \text{ V} - 0.7 \text{ V}}{31.25 \mu\text{A}}$$

$$= 361.6 \text{ k}\Omega \rightarrow \text{Ans.}$$

$$R_C = \frac{V_{RC}}{I_C} = \frac{V_{CC} - V_C}{I_C} = \frac{V_{CC} - V_{CEQ}}{I_{CQ}}$$

$$= \frac{12 \text{ V} - 6 \text{ V}}{2.5 \text{ mA}} = 2.4 \text{ k}\Omega \rightarrow \text{Ans.}$$

8. **D. collector-base**

9. **D. 1.52 mA**

Solution:

$$I_E = \frac{I_C - I_{CEO}}{\alpha}$$

$$I_E = \frac{1.5 \text{ mA} - 1 \mu\text{A}}{0.984}$$

$$I_E = 1.52 \text{ mA} \rightarrow \text{Ans.}$$

where :

$$\alpha = \frac{\beta}{1 + \beta} = \frac{60}{1 + 60}$$

$$\alpha = 0.984$$

10. **D. hold the circuit stable at the designed Q-point**

11. **B. 4 mW**

Solution:

$$P_{D(\text{ave})} = \left(\frac{t_{\text{on}}}{T} \right) V_{CE(\text{sat})} I_{C(\text{sat})}$$

$$= \left(\frac{1 \mu\text{s}}{5 \mu\text{s}} \right) (0.2 \text{ V})(100 \text{ mA})$$

$$P_{D(\text{ave})} = 4 \text{ mW} \rightarrow \text{Ans}$$

12. **C. I_C and I_E .**

13. **A. saturation and cutoff**

14. **A. the common-emitter amplifier.**

15. **A. the emitter region.**

16. **A. 2.78 mA**

Solution:

$$I_E = I_C + I_B$$

$$I_C = I_E - I_B$$

$$I_C = 2.8 \text{ mA} - 0.02 \text{ mA}$$

$$I_C = 2.78 \text{ mA} \rightarrow \text{Ans.}$$

17. **C. 0.7 V across each depletion layer**

18. **D. the base region.**

19. **D. Both A and C.**

20. **D. base bias.**

21. **C. $V_{CE} = 0 \text{ V}$.**

22. **B. $V_{CE} = V_{CC}$.**

23. **B. 3.992 mA**

Solution:

$$I_C = \alpha I_E = (0.998)(4 \text{ mA})$$

$$I_C = 3.992 \text{ mA} \rightarrow \text{Ans.}$$

24. **A. crossover distortion**

25. **B. The emitter follower**

26. **A. stabilization**

27. **A. 3.25 mA**

Solution:

$$\alpha = \frac{I_{CQ}}{I_{EQ}}$$

$$I_{EQ} = \frac{I_{CQ}}{\alpha} = \frac{3.12 \text{ mA}}{0.96}$$

$$= 3.25 \text{ mA} \rightarrow \text{Ans.}$$

where :

$$I_{CQ} = \beta I_{BQ(\text{act.})} = (24)(130 \times 10^{-6})$$

$$I_{CQ} = 3.12 \text{ mA}$$

$$I_{BQ(\text{act.})} = I_{BQ} + I_{CBQ} = 120 \mu\text{A} + 10 \mu\text{A}$$

$$I_{BQ(\text{act.})} = 130 \mu\text{A}$$

$$\beta = \frac{\alpha}{1 - \alpha} = \frac{0.96}{1 - 0.96} = 24$$

28. **D. its low input impedance.**

29. **B. collector is positive with respect to base**

30. **A. the active region.**

31. **B. the collector region.**

32. **C. The common-emitter amplifier**

33. **A. A_v decreases.**

34. **A. The common-base amplifier**

35. **B. the common-collector amplifier.**

36. **B. Active region**

37. **B. $I_{C(\text{Sat})}$ and $V_{CE(\text{off})}$.**

38. **A. Forward bias the base/emitter junction and reverse bias the base/collector junction.**

39. **A. I_C/I_E .**

40. **A. The common-base amplifier**

41. **C. V_c decreases.**



- 42. **A. cut off.**
- 43. **D. Both A and B.**
- 44. **C. low resistance**
- 45. **D. two p-n junctions.**
- 46. **B. very stable Q point.**
- 47. **D. Both A and B.**
- 48. **C. emitter current**
- 49. **A. the common-collector amplifier.**
- 50. **C. collector current and collector to emitter voltage**

END

