



Answers:

- | | | |
|---|--|--|
| <p>1. C. Obtain an instruction</p> <p>2. C. Has a high impedance state in addition to normal 0 and 1 levels</p> <p>3. B. Present as well as past inputs</p> <p>4. B. As long as power is applied to the memory</p> <p>5. A. Similar points on the clock waveform</p> <p>6. A. To make a transition from a low level to a high level</p> <p>7. B. Sample and display system signals</p> <p>8. A. HIGH</p> <p>9. B. input terminals</p> <p>10. A. lower propagation delay</p> <p>11. D. B and C above</p> <p>12. A. makes logic decision</p> <p>13. B. NOR</p> <p>14. B. Data must be held on the input after a clock edge</p> <p>15. D. OFF</p> <p>16. C. Shannon</p> <p>17. B. different</p> <p>18. D. only such don't cares that aid minimization are treated as logic 1s</p> <p>19. C. logic</p> <p>20. D. multiemitter transistor</p> <p>21. D. All of these</p> <p>22. A. A binary input select code</p> <p>23. D. Both row and column decoders</p> | <p>24. D. cause the output to assume a state dependent on the controlling inputs</p> <p>25. D. AND</p> <p>26. C. one XOR and one OR gate with their inputs connected in parallel</p> <p>27. A. very high speed</p> <p>28. C. at the same logic level</p> <p>29. D. Any of the above</p> <p>30. C. 10% to 90% points on the voltage transition</p> <p>31. D. Is the central control element of the system</p> <p>32. C. As long as power is applied and the memory is refreshed periodically</p> <p>33. B. The output enable must be true</p> <p>34. B. $A.0 = 0$</p> <p>35. B. power dissipation in nanowatt range</p> <p>36. B. 2</p> <p>37. C. Clock must be high</p> <p>38. C. Monostable multivibrator</p> <p>39. C. 1000</p> <p>40. B. 8</p> <p>41. C. bistable multivibrators</p> <p>42. A. A</p> <p>43. D. $S=0, C=0$</p> <p>44. C. To get information into, act on it, and output it from the system</p> <p>45. A. much reduced power</p> <p>46. B. Row decoders</p> | <p>47. D. Data must be stable prior to a clock edge</p> <p>48. B. S-C flip-flop</p> <p>49. B. propagation delay</p> <p>50. C. Provides an output code that corresponds to which of a set of input lines is true</p> <p>END</p> |
|---|--|--|